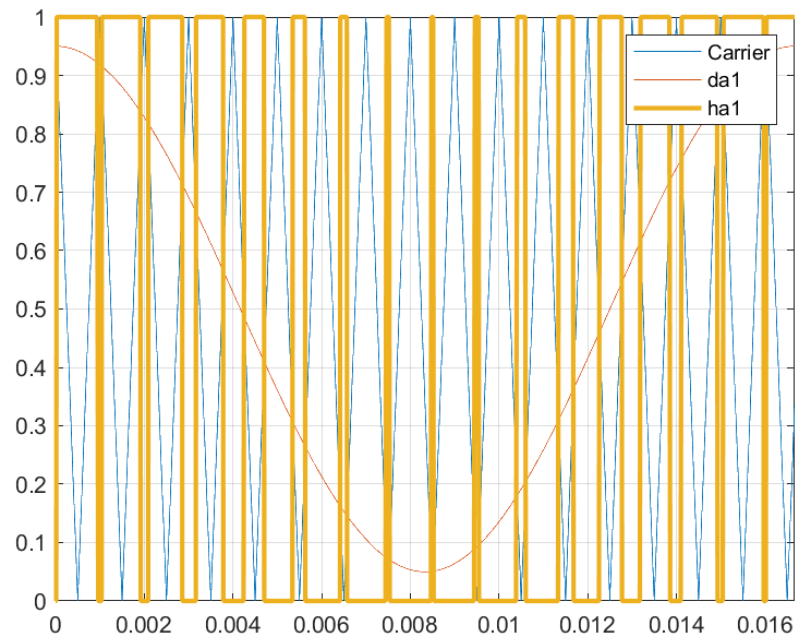



Hyeongmeen Baik

ALE 3

**Part a.** Plot  $d_{a1}(t)$ , carrier(t), and  $h_{a1}(t)$  on the same plot for one fundamental (60 Hz) period, for  $T_s = 1/f_s = (1/1000)$  s. Make sure the index of your time array is  $< T_s/30$ , and ideally  $< T_s/100$



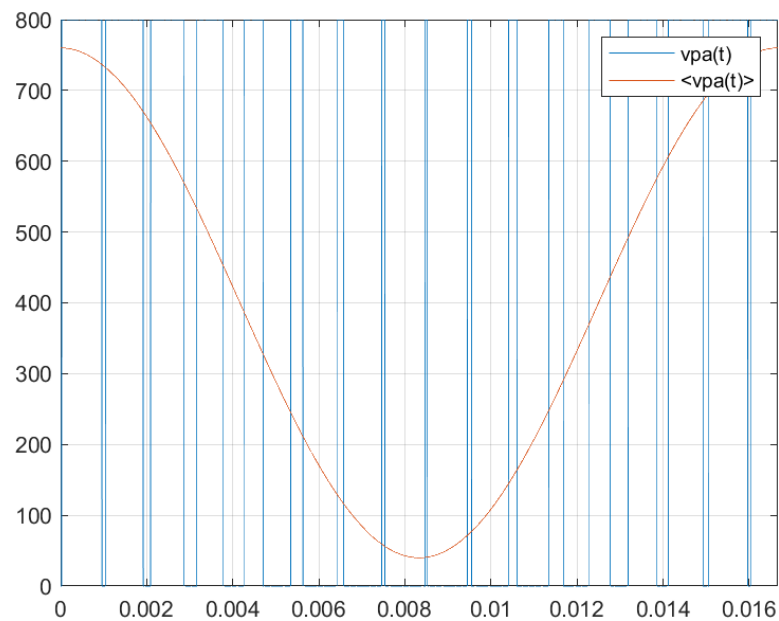
**Part b.** If the dc bus is 800V, plot the instantaneous pole voltage,  $v_{pa}(t)$  and short time average  $\langle v_{pa}(t) \rangle$ . What is the maximum voltage rating that devices in the 1P2T will need to block?




The maximum blocking voltage is 800V, when the other switch is operating.

**Part c.** If the pole current is  $i_{pa}(t) = 30 \cos(\omega t - \frac{\pi}{3})$ , plot the following on the same graph.

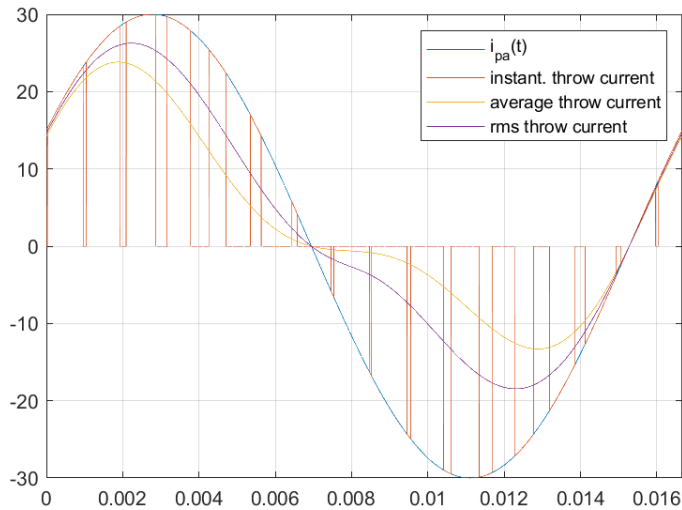- 1: pole current =  $i_{pa}(t)$
- 2: instantaneous throw current  $h_{a1}(t) * i_{pa}(t)$
- 3: average throw current =  $d_{a1}(t) * i_{pa}(t)$
- 4: rms throw current =  $\sqrt{d_{a1}(t) * i_{pa}(t)}$



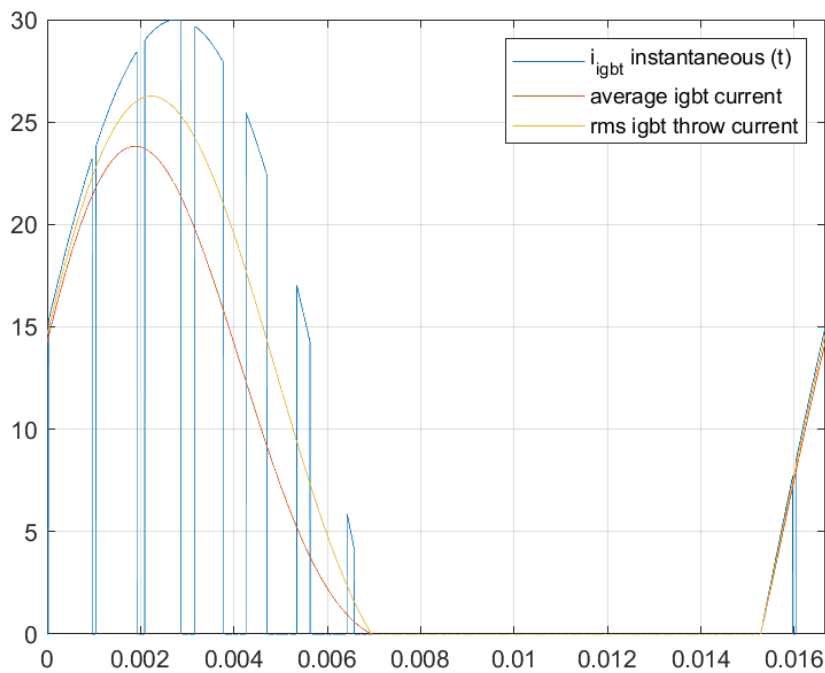**Part d.** If the upper pair of devices is an IGBT and diode, what is the IGBT's instantaneous, average and RMS currents? Plot these along with  $i_{pa}(t)$ .



**Part e.** (Optional) Plot the upper throw diode currents (instantaneous, average and RMS).

